



# Design of RTD Signal Conditioning Circuit

## GROUP1

SHUBHANKAR JOSHI -18

YOGESH KADAM -20

VARAD KAJAREKAR -22

KRUNAL KALE -24

JAYESH KAMANE -25

# Objective

- ▶ To design a signal conditioning circuit for RTD.
  - ▶ Task 1 – For 0 C output is 0V and for 100 C output is 5V
  - ▶ Task 2 – For 25 C output is 0V and for 100 C output is 5V

# Individual Problem Statement

- ▶ Varad Kajarekar – Worked on Task 1
- ▶ Yogesh Kadam - Worked on Task 1
- ▶ Krunal Kale - Calculation work
- ▶ Shubhankar Joshi - Worked on Task 2
- ▶ Jayesh Kamane - Worked on Task 2

# Introduction

- ▶ RTDs, or resistance temperature detectors, are sensors used to measure temperature.
- ▶ These sensors are among the most accurate temperature sensors available, covering large temperature ranges.

The variation of resistance of the metal with the variation of the temperature is given as,

$$R_T = R_{ref} [1 + \alpha (T - T_{ref})]$$

- ▶ Where,  $R_t$  and  $R_0$  are the resistance values at  $t^\circ\text{C}$  and  $t_0^\circ\text{C}$  temperatures.  $\alpha$  and  $\beta$  are the constants depends on the metals.




# Wheatstone Bridge

- ▶ The Wheatstone Bridge diamond shaped circuit who's concept was developed by Charles Wheatstone can be used to accurately measure unknown resistance values, or as a means of calibrating measuring instruments, voltmeters, ammeters, etc, by the use of a variable resistance and a simple mathematical formula.

$$V_C = \frac{R_2}{(R_1 + R_2)} \times V_S$$

$$V_D = \frac{R_4}{(R_3 + R_4)} \times V_S$$


$$V_{OUT} = V_C - V_D$$

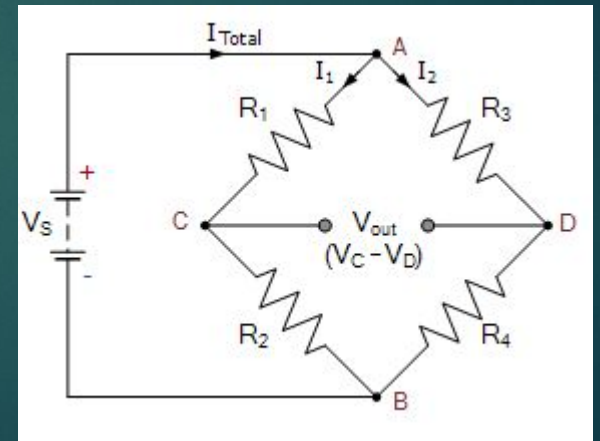
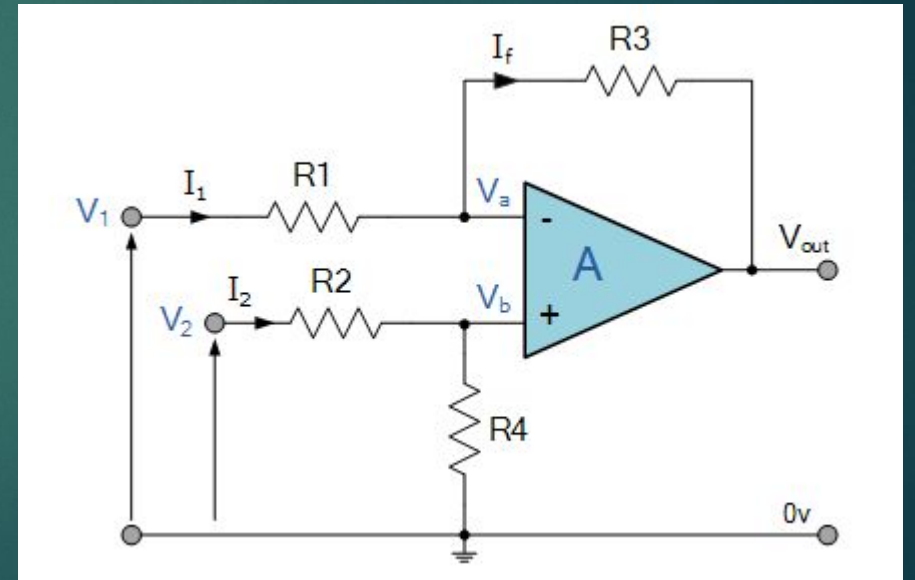
# Differential Amplifier

- ▶ A differential amplifier is a type of electronic amplifier that amplifies the difference between two input voltages but suppresses any voltage common to the two inputs


$$V_{OUT} = \frac{R_3}{R_1} (V_2 - V_1)$$



# Non-Inverting Opamp

- A non-inverting op amp is an operational amplifier circuit with an output voltage that is in phase with the input voltage.

$$A_{(v)} = 1 + \frac{R_F}{R_2}$$

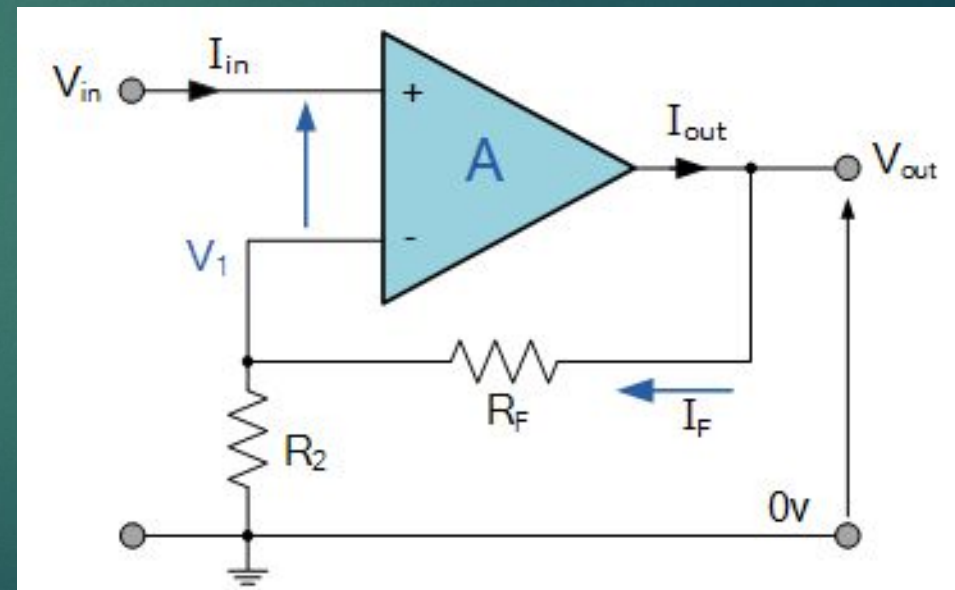




# Circuit Diagram

$$V_{OUT} = \frac{R_3}{R_1} (V_2 - V_1)$$

$$A_{(v)} = 1 + \frac{R_F}{R_2}$$

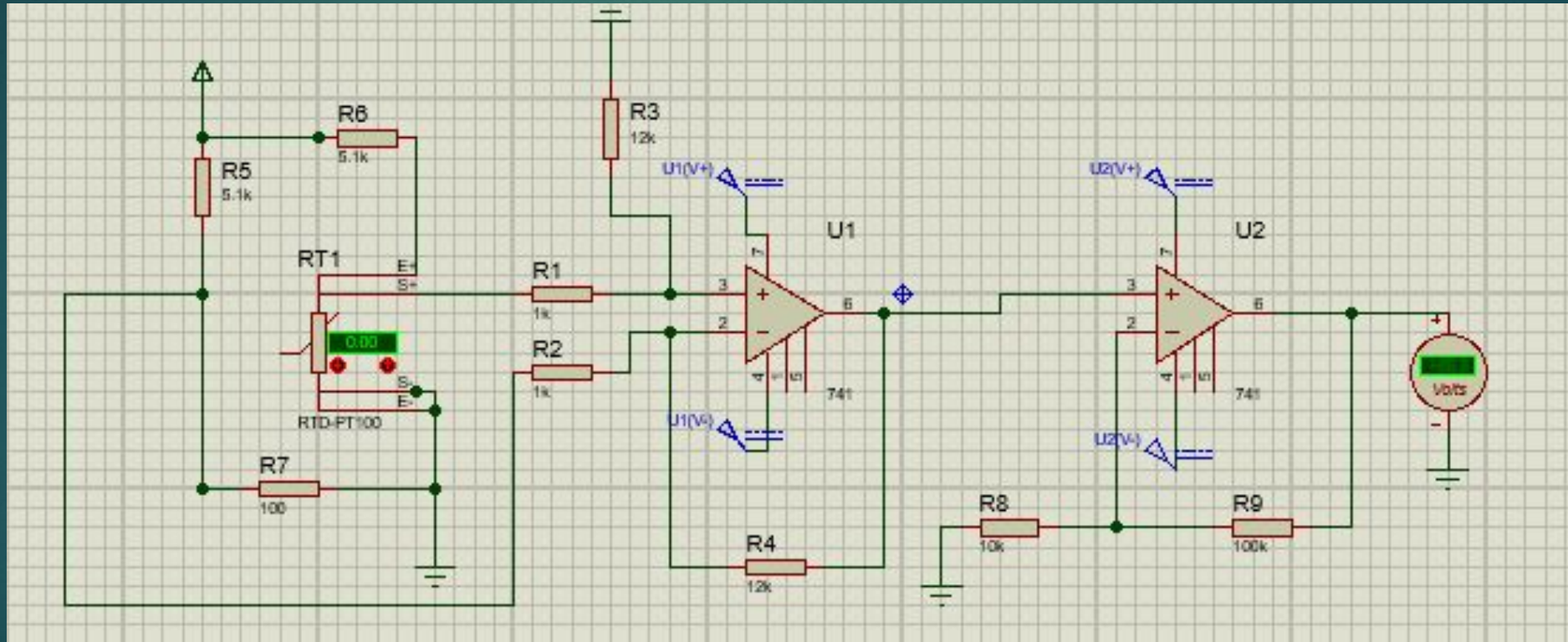



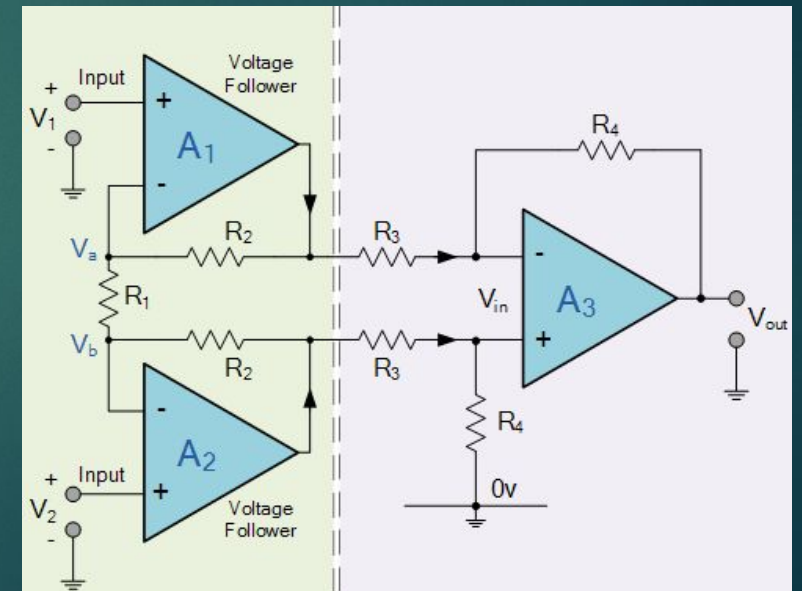
# Instrumentation Amplifier

- ▶ Instrumentation Amplifiers (in-amps) are very high gain differential amplifiers which have a high input impedance and a single ended output. Instrumentation amplifiers are mainly used to amplify very small differential signals from strain gauges, thermocouples or current sensing devices in motor control systems.

$$V_{OUT} = (V_2 - V_1) \left[ 1 + \frac{2R_2}{R_1} \right] \left( \frac{R_4}{R_3} \right)$$



# Circuit diagram

